
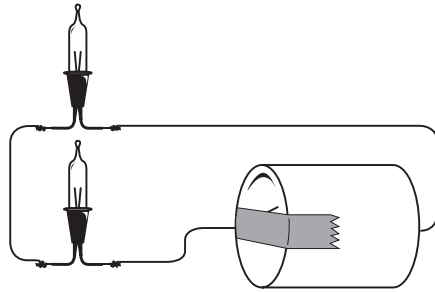


### ELECTRIC CIRCUITS WORKSHEET

#### Part 2: Dimmer and Brighter

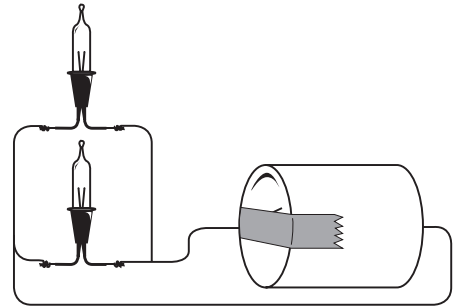

Circuit A



Circuit B

#### Circuit A

Intensity of the light bulbs:      dim                      bright

What happens when one of the bulbs is removed? .....

.....

.....

.....

.....

#### Circuit B

Intensity of the light bulbs:      dim                      bright

What happens when one of the bulbs is removed? .....

.....

.....

.....

.....

With your team, brainstorm reasons why the answers in circuits A and B would be different.

.....

.....

.....

.....